

# REMOTELY CONTROLLED STAGING/INTERCHANGE

Mike Barrett

September 12, 2020

Div 4 ZOOM


ABSTRACT - This is a description of how a remote staging, or interchange, yard can be built and operated in a hands-off fashion. Track selection is performed by pushbutton. Uncoupling is accomplished with Kadee electromagnetic coils that are controlled by an Arduino. Coupling and uncoupling are facilitated by "bumper cars" that provide resistance for coupling, and an anchor when cars are uncoupled.


Highlights:

- Pushbutton track selection
- Kadee uncoupling coil with timed activation controlled by Arduino
- Bumper cars aid coupling and uncoupling

# Mopac Interchange

Mopac access track

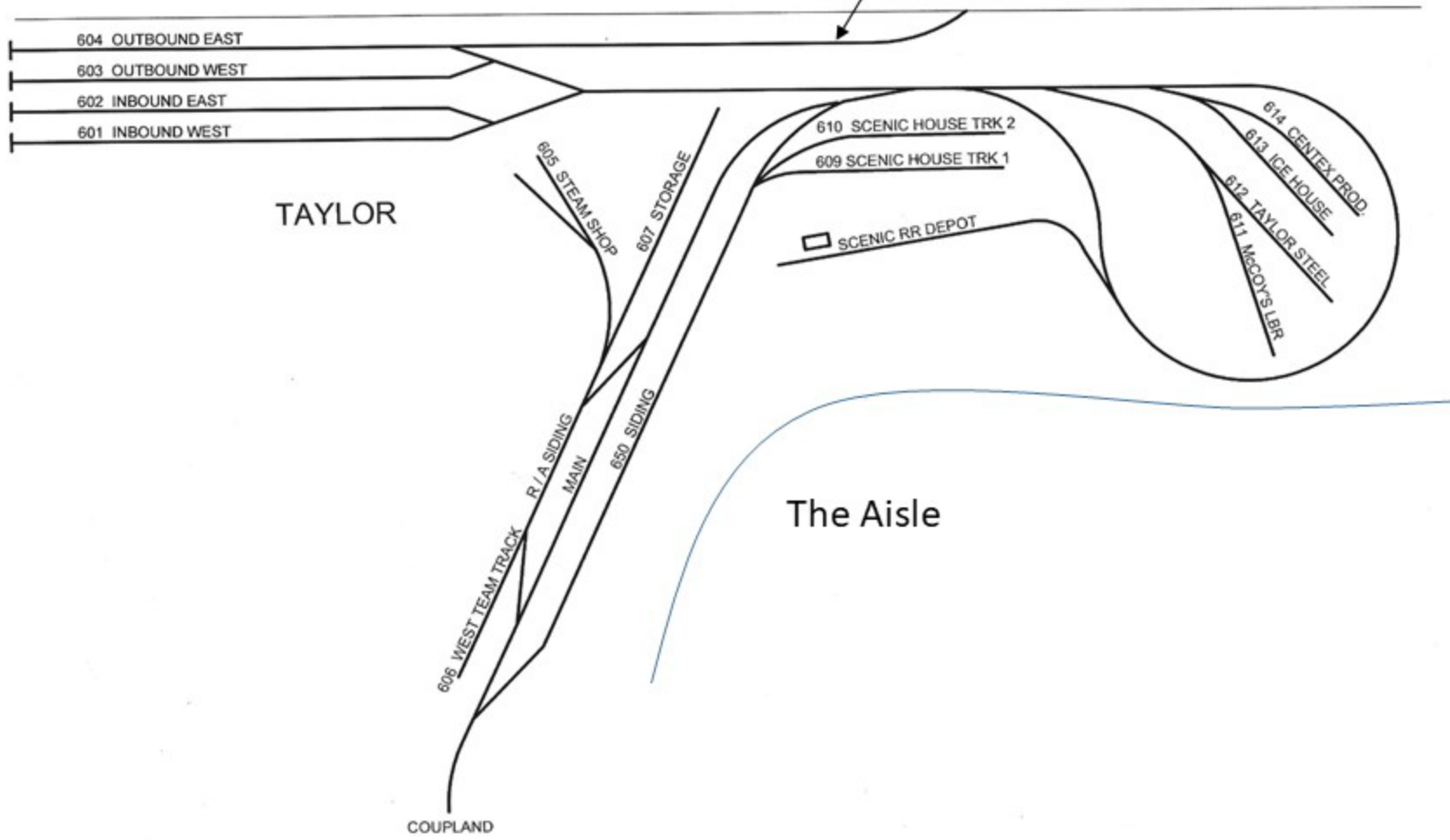

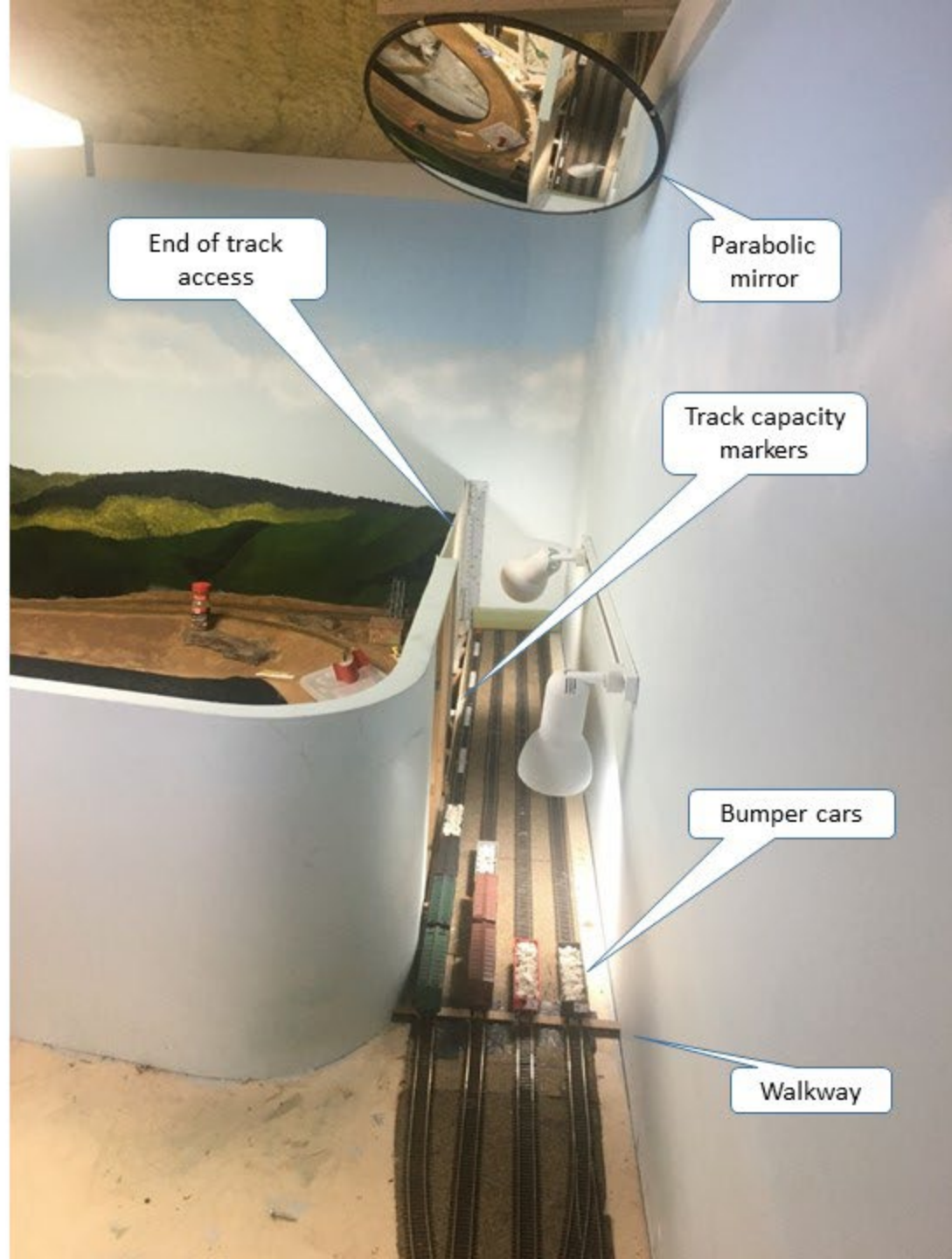


End of track  
access

Parabolic  
mirror

Track capacity  
markers

Bumper cars

Walkway

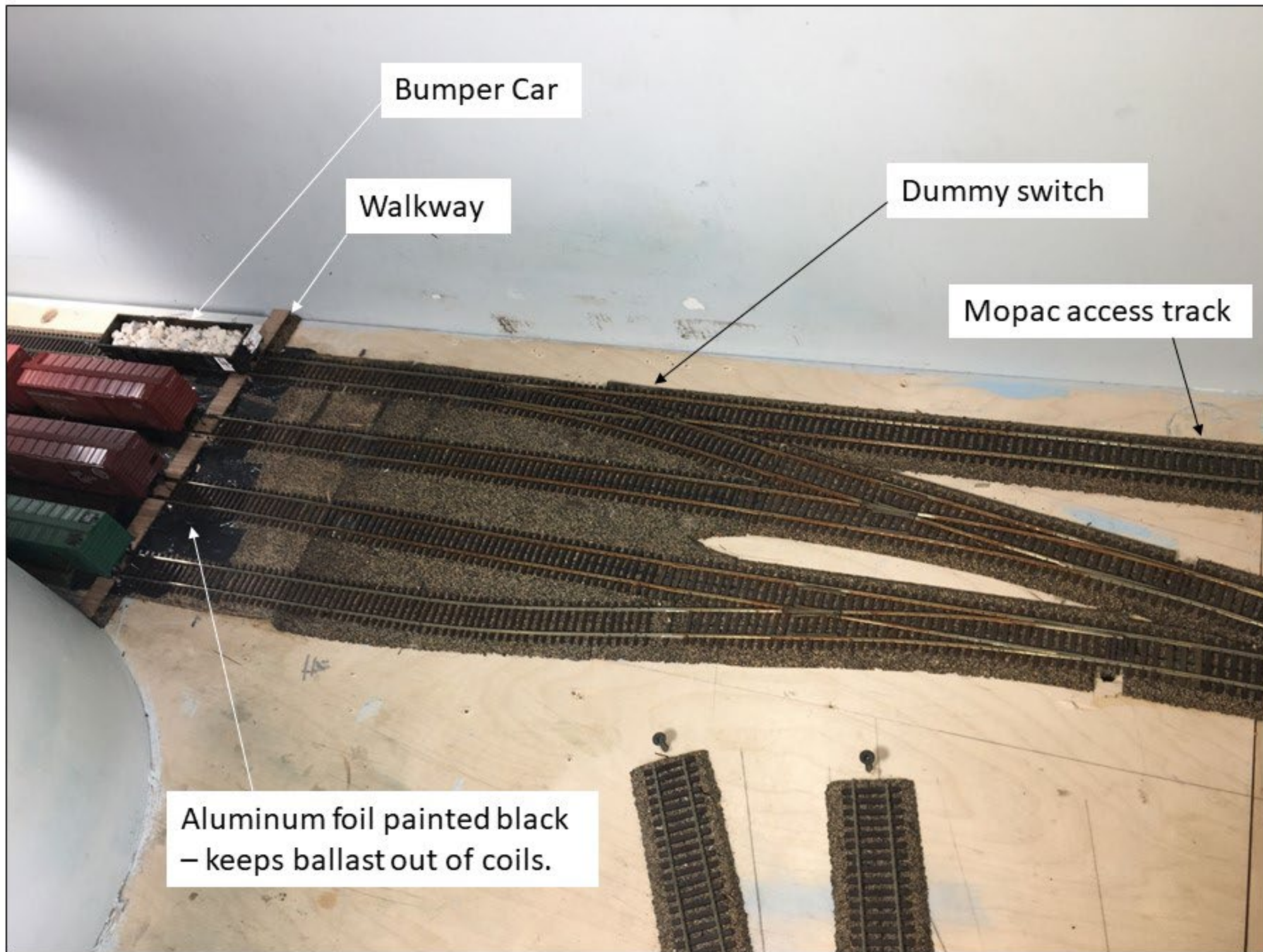

Bumper Car

Walkway


Dummy switch

Mopac access track

Aluminum foil painted black  
- keeps ballast out of coils.



# Bumper Cars

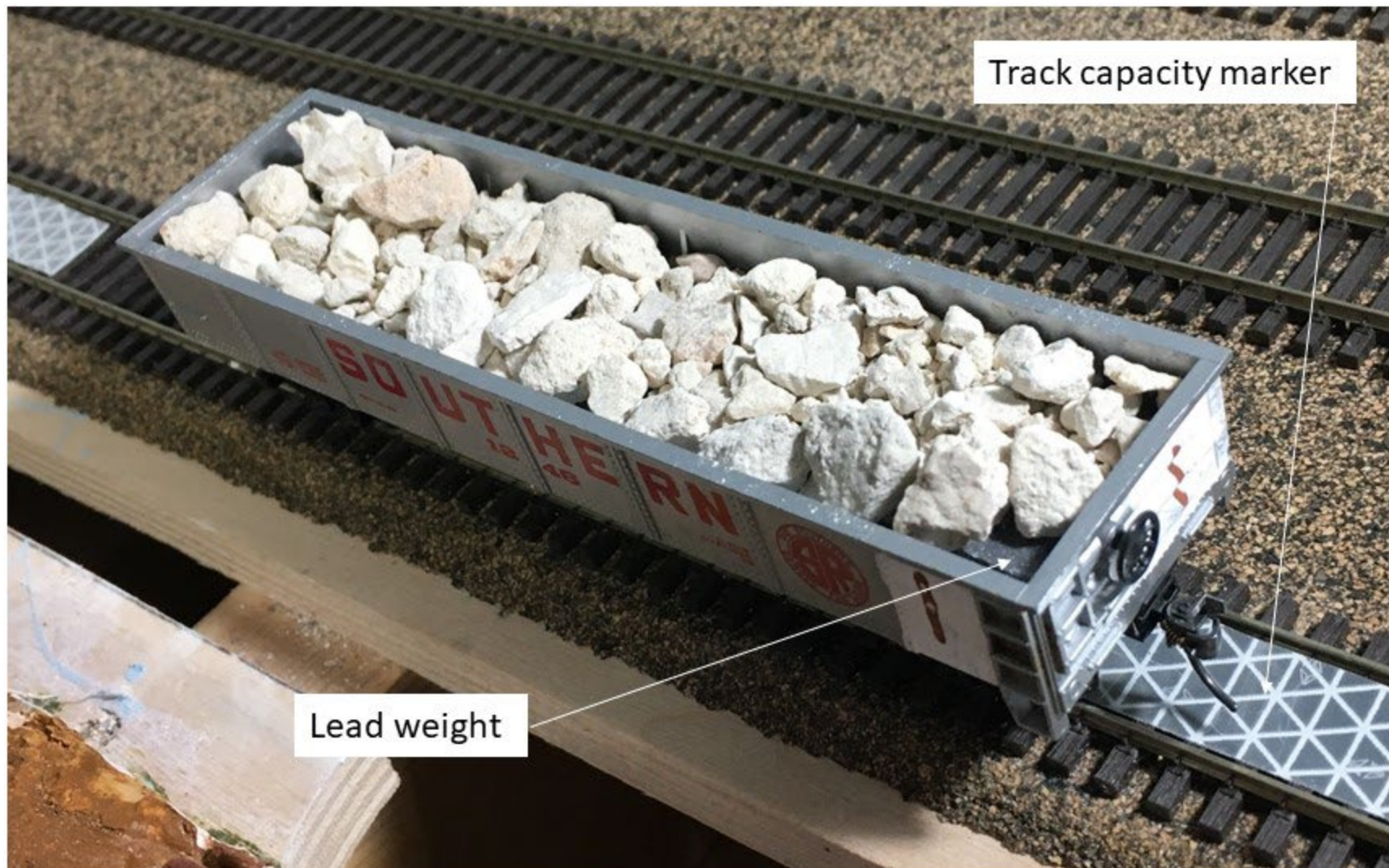

Wood spacers



Tortoise switch machine

Tortoise Buddy Wiz-Kid

Switching controlled by pulse


Contact closures indicate switch direction




Connector J7


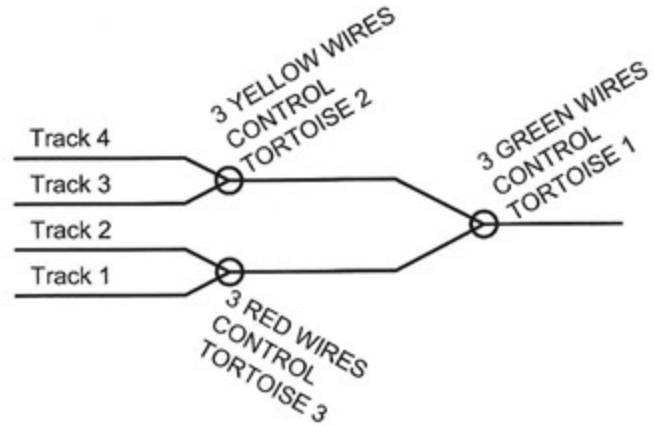
# CONTROLLING TRACK SELECTION WITH DPST PUSHBUTTONS



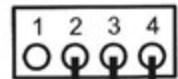
CONNECTIONS TO TORTOISE  
BUDDY WIZ-KID  
Connector J7  
Switch Control




Tape Color  
red, white, or blue

Wire color  
YELLOW, GREEN, RED

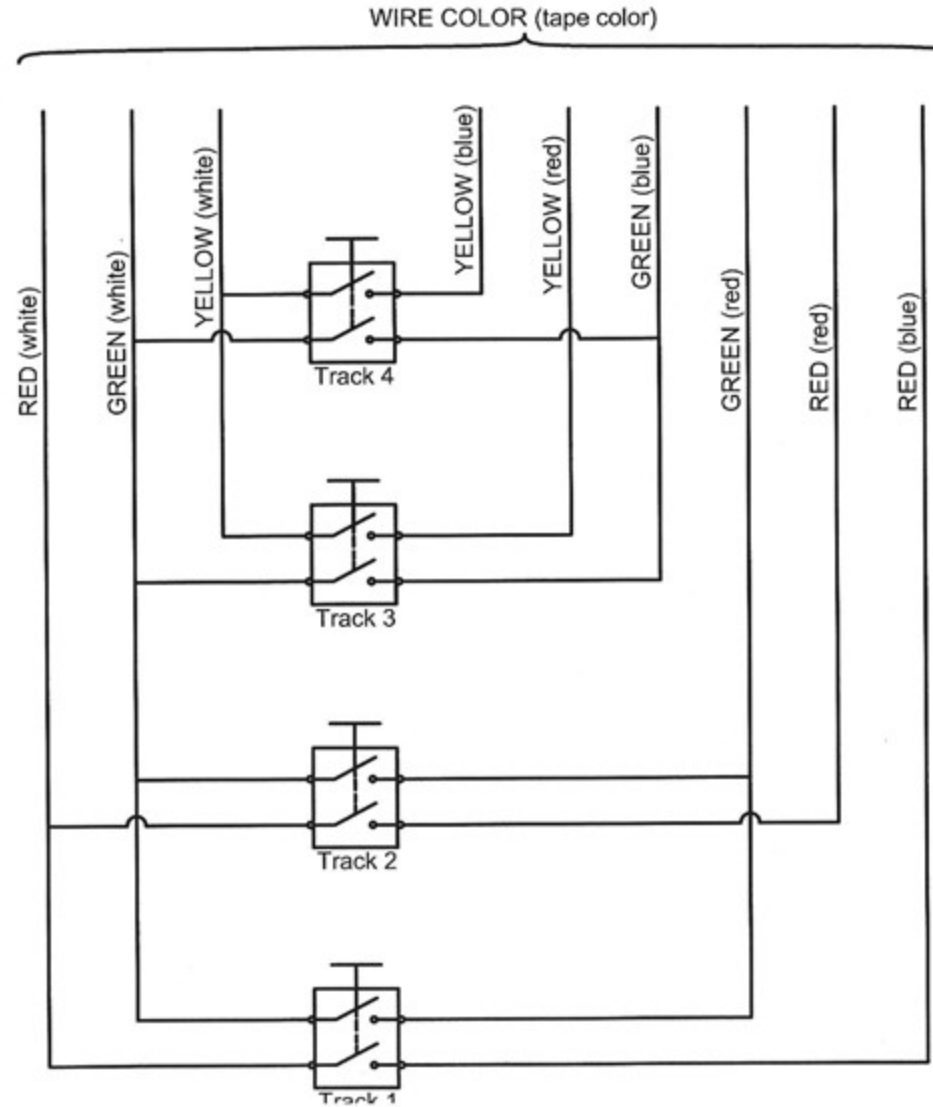Short contacts 2 and 3, switch goes one way.  
Short contacts 3 and 4, switch goes other way.




# CONTROL PANEL LED's INDICATE THE TRACK


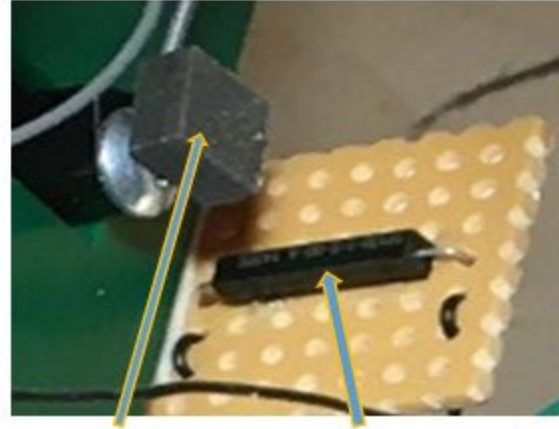


Permanent magnet


Reed switch  
(200V, .5A)

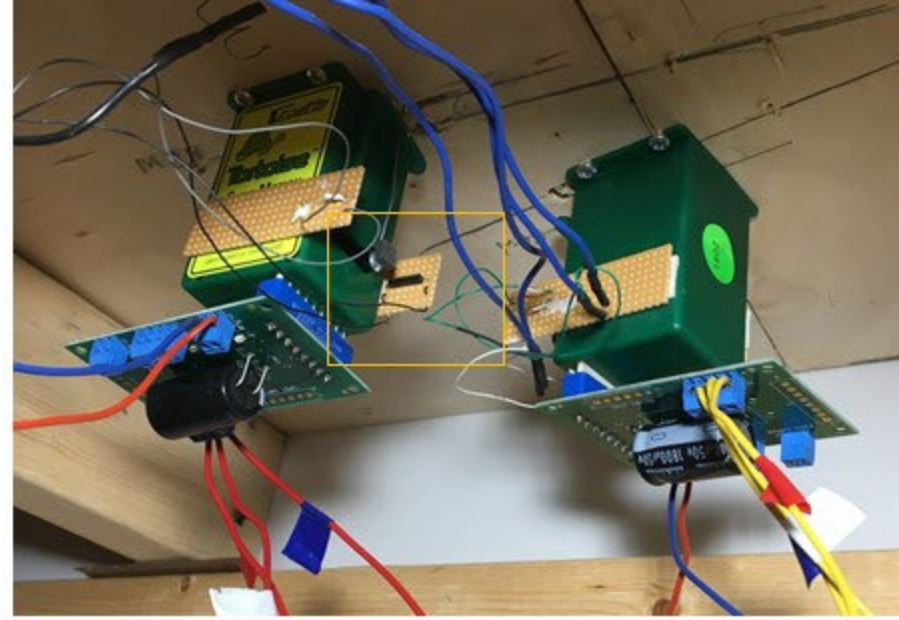

## HOW REED SWITCHES WORK

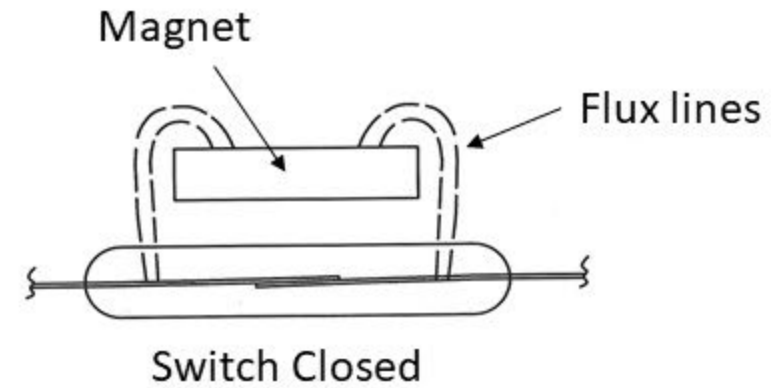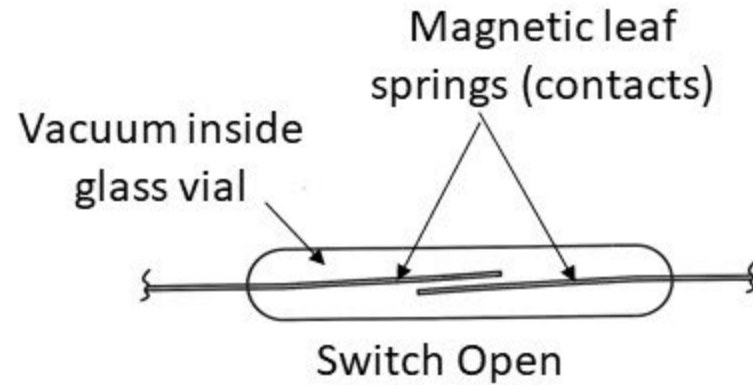


# LIGHTING UP THE RIGHT LED

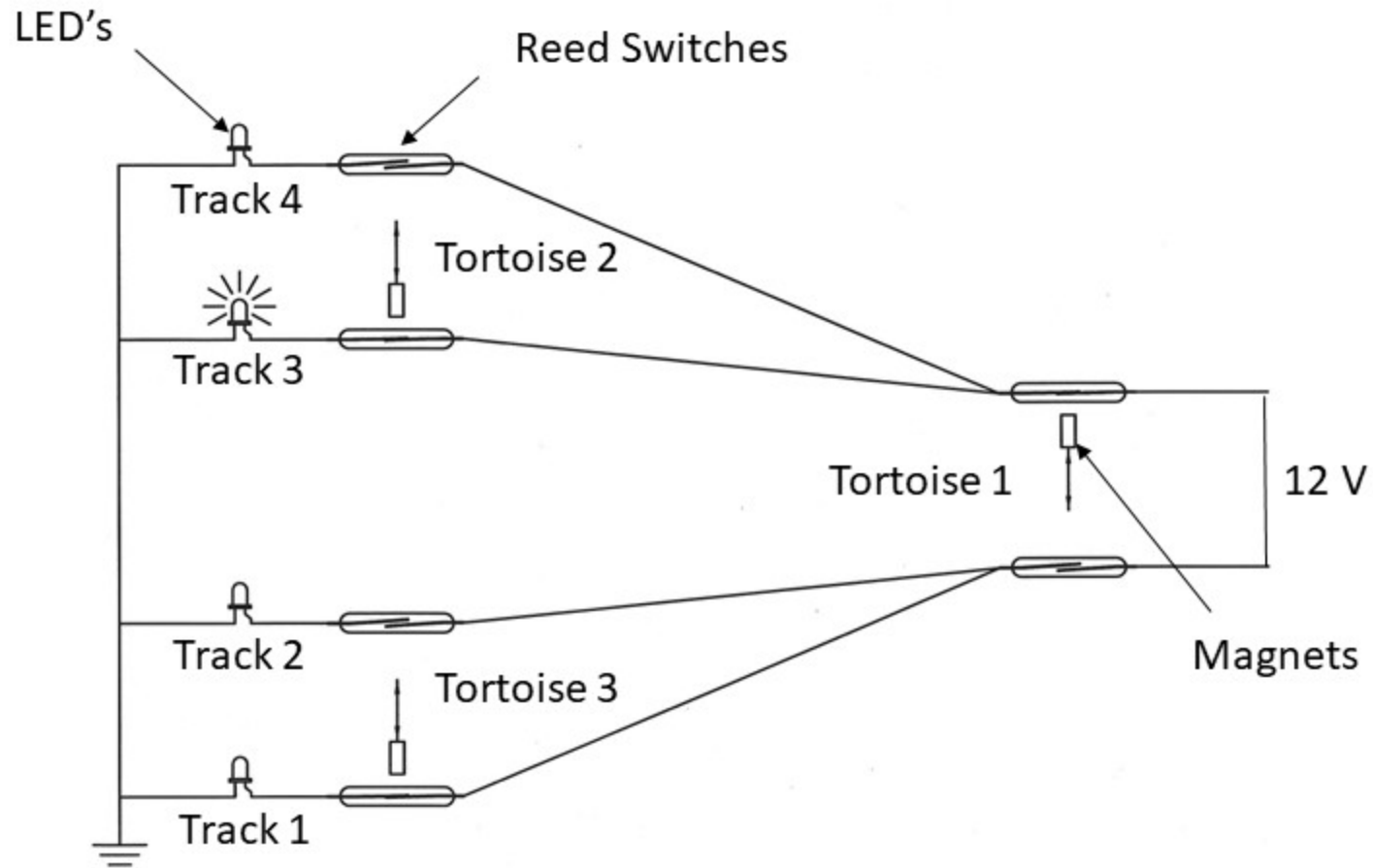

Tortoises are lined up on track 3, so light up track 3 LED.

# Control Panel

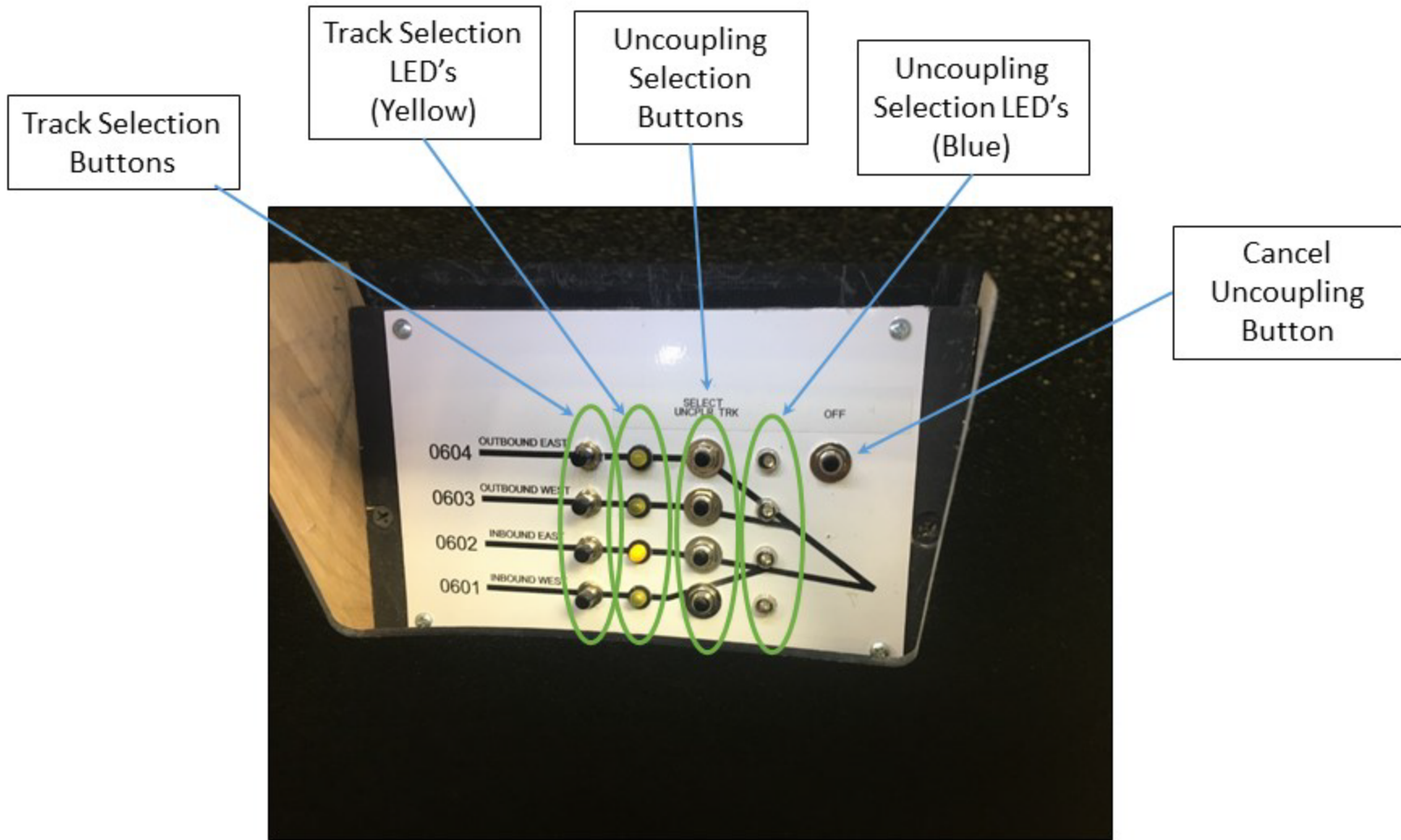




Selected track is indicated  
with yellow LED




# UNCOUPLING
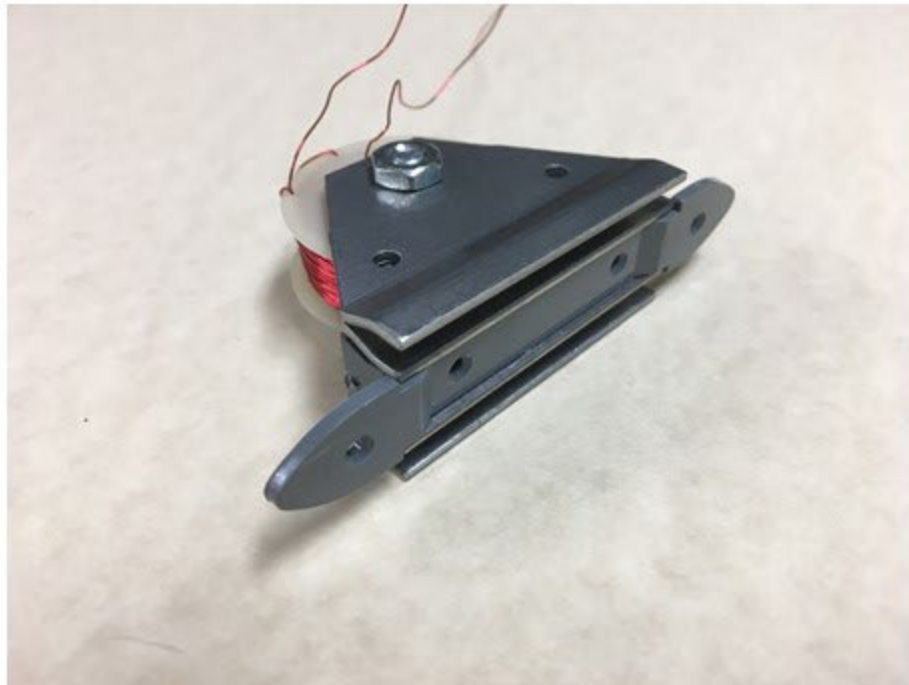
## KADEE 309 Electromagnetic Uncoupler

- “Why not?” other uncouplers
- Spontaneous uncoupling
  - Spotting accuracy
  - Electrical noise (?)
  - Delayed uncoupling can fail



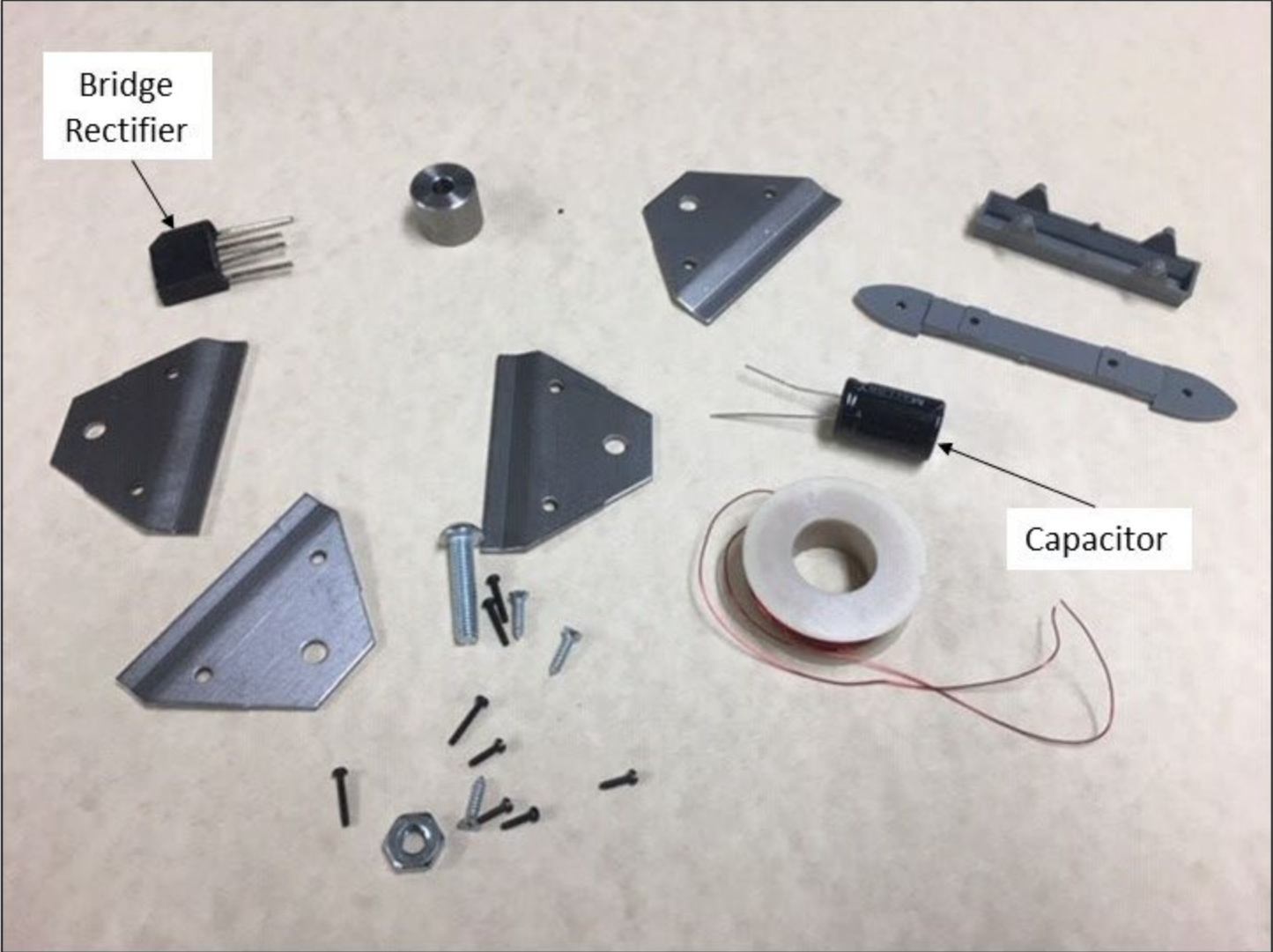

Bridge  
Rectifier

Capacitor

Coil assembly is attached  
to a piece of track.



Under The Ties 309

DELAYED-ACTION

MAGNE-ELECTRIC UNCOUPLER

### ASSEMBLY INSTRUCTIONS

**BEFORE YOU BEGIN CAREFULLY READ THE INSTRUCTIONS AND STUDY THE ILLUSTRATIONS.** Check the package contents and familiarize yourself with each part. If any parts are missing, damaged, or defective please contact Kadee® Quality Products at the address on the package.

**PACKAGE CONTENTS:** 1 each of the following: coil, steel core, bolt and hex nut, field plate divider, upper track mounting plate, bridge rectifier, radial capacitor, 4 each field plates, 3 each 2-56 flat head screws, 4 each 0-48 x 3/8" screws, 4 each 0-48 x 1/4" screws.

### OTHER ITEMS NEEDED:

These are to be provided by the modeler. 16 volt DC power source (at least 1.5 Amps) or 18 volt AC power source (at least 1.5 Amps) converted to DC with bridge rectifier. The Kadee® #166 Transformer meets power requirements, small piece of aluminum foil for ballast, #52 and #55 drill bits, (Kadee® #780 Tap & Drill set) 20 gauge wire, Kadee® #165 Normally Open momentary contact push button switch, light bulbs or LEDs of appropriate voltage, AMP/ Voltage meter, general hobby tools, wood working tools for cutting a hole into the layout base (see text) and tools to cut the

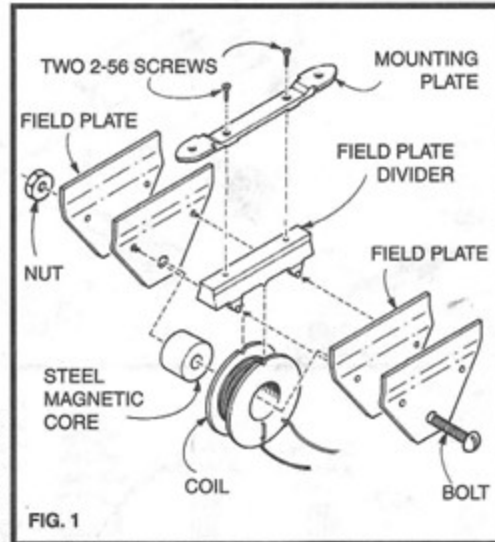


FIG. 1

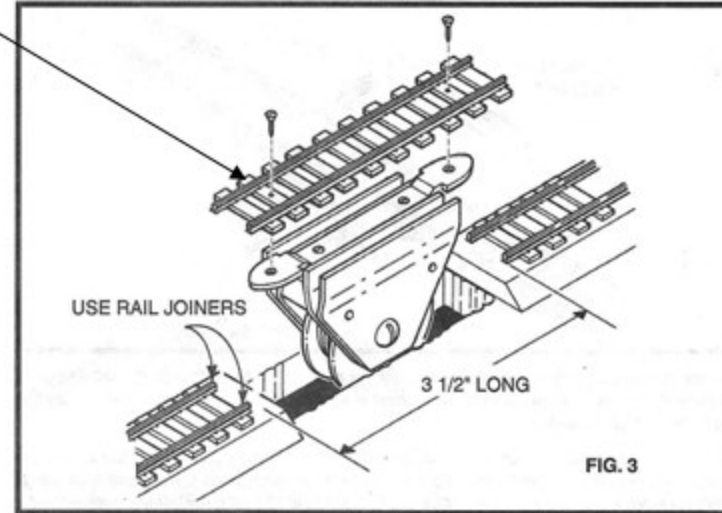


FIG. 3

To avoid overheating and to assure reliable operation the uncoupler must have an electrical source of at least 3 Amps and no more than 16 volts DC. **Do not energize continuously for more than two minutes, or overheating will occur.**

**ASSEMBLY & INSTALLATION:** It would be best, where possible, to install the #309 uncoupler while you are building your layout. All uncouplers should be placed on a straight piece of track where your two longest models will fit on each side of the uncoupler. We do "not" recommend placing an uncoupler on or near a curve, switch, or turn out, both models need to be as straight as possible with each other for reliable uncoupling.


Assemble the uncoupler as the illustration shows (fig. #1). Insert the core into the coil, fit two field plates opposite to each other, one bent out one bent inward, as shown, slip the bolt through, place the field plate divider into the holes of the field plate, fit the other field plates over the bolt and against the coil. Make sure the prongs on the divider are inserted into the holes on the field plates and the tabs are fitted into notches of the coil where the lead wires are at the bottom of the coil and not under the field plates. Place the hex nut onto the bolt and tighten just snug and turn the assembly upside-down and tap it on a flat surface to get the plates aligned as even as possible, hold it on the surface and tighten the hex nut firmly. Set the top plate onto the divider (between the field plates) and secure with the 2-56 flathead screws, tighten just firm, overtightening will easily strip the plastic holes.

After you have determined the location where you wish to install the uncoupler you will have to cut a hole in the layout surface (base). The hole must be 1-1/16" wide and 2-1/8"

16 V, 1.6 A



## Arduino – Mega 2560

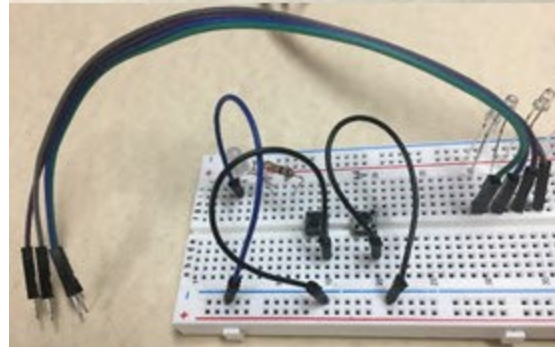

Combine an  
Arduino and a  
breadboard

# ...RRduino...

by Speed

In the current Marker Lamp

```
#define RELAYOUT01 40
#define RELAYOUT02 42
#define RELAYOUT03 44
#define RELAYOUT04 46
#define LED01 32
#define LED02 34
#define LED03 36
#define LED04 38
#define BUTTONIN01 22
#define BUTTONIN02 24
#define BUTTONIN03 26
#define BUTTONIN04 28
#define BUTTONIN05 30
#define LEDPIN 13
```

Assign variable names to pins

```
// TIMEOUT is in milliseconds, so 10 seconds is 10,000 milliseconds
#define TIMEOUT 5000 // relay turns off after...5 seconds
#define LEDTOGGLE 200 // cycle period of pin 13
```

Define uncoupling duration as 5 seconds

Turn LED and Relay OFF  
if 5 seconds exceeded


```
void loop() { // Loop starts here
  now = millis(); // capture now

  // first relay
  if( relayOn01 ) { // is relay01 on? then check timeout
    if ( now - beforeRelay01 > TIMEOUT ) { // now minus before longer than timeout?
      digitalWrite( LED01, HIGH ); // turn LED off
      digitalWrite( RELAYOUT01, HIGH ); // turn relay off
      relayOn01 = false; // no need to check for timeout, since it is now off
    } // if timeout
  } // if on
```


Turn LED and Relay ON  
if button pushed


```
if( digitalRead( BUTTONIN01 ) == LOW ) { // the button is connected to ground when pressed, thus LOW
  allOff();
  relayOn01 = true; // now we should check the timeout
  beforeRelay01 = now; // set the time to check against
  digitalWrite( LED01, LOW ); // turn LED on
  digitalWrite( RELAYOUT01, LOW ); // turn relay on
} // if pressed
```

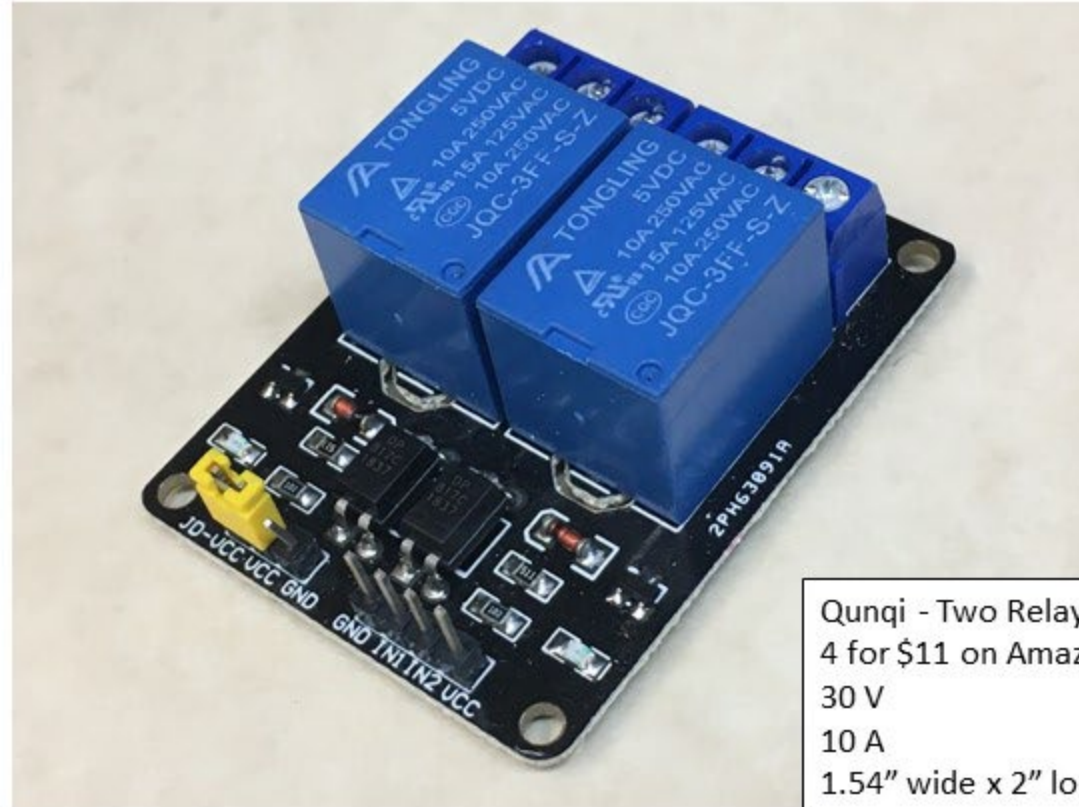Coil is energized by an Arduino turning on a powerful relay.




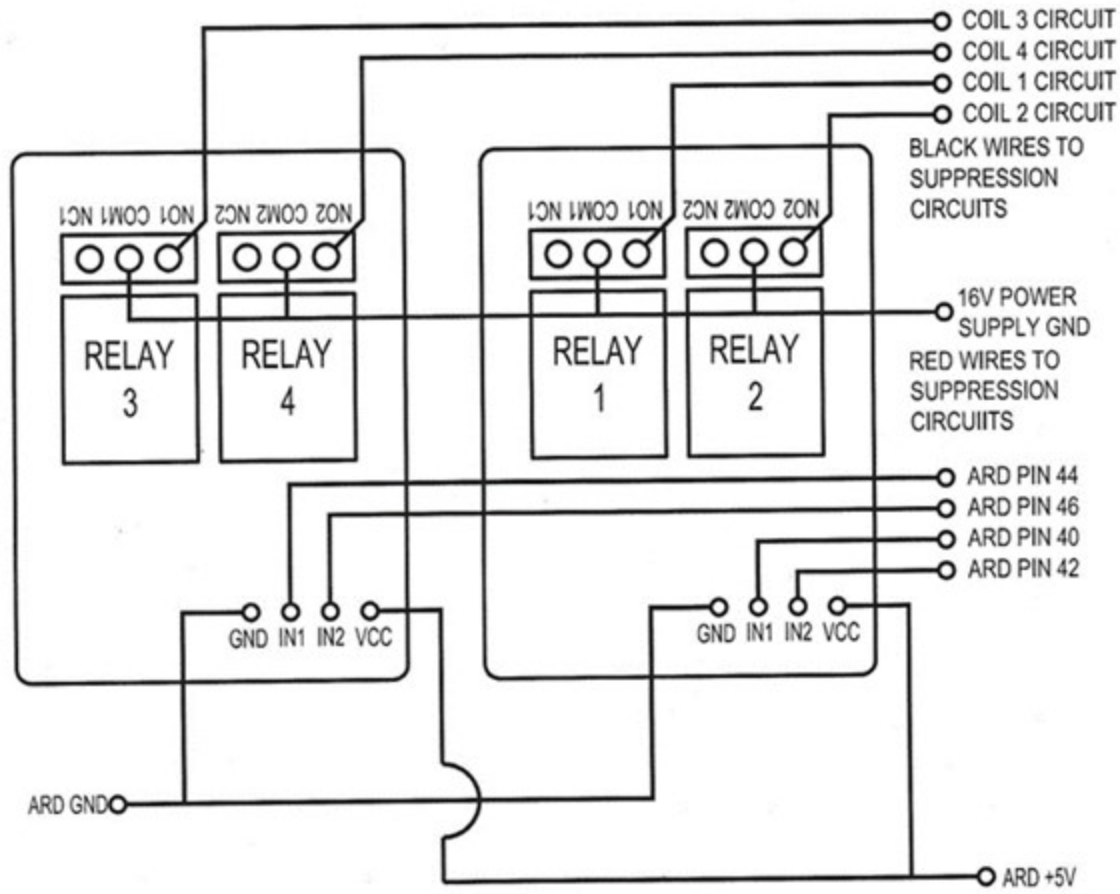
Qunqi - Two Relays  
4 for \$11 on Amazon  
30 V  
10 A  
1.54" wide x 2" long x .75" tall



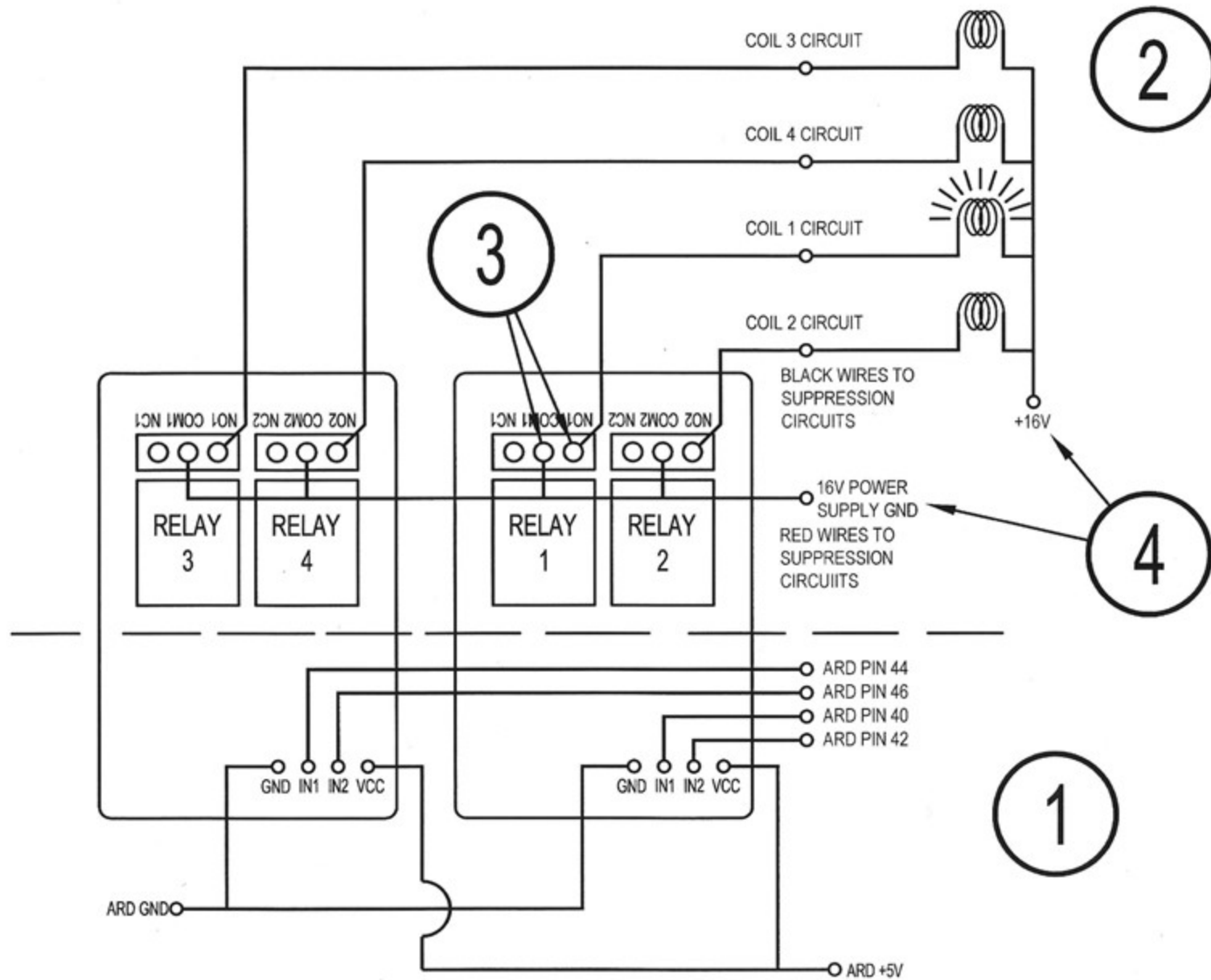

And one more thing . . .

## An energy dissipation circuit

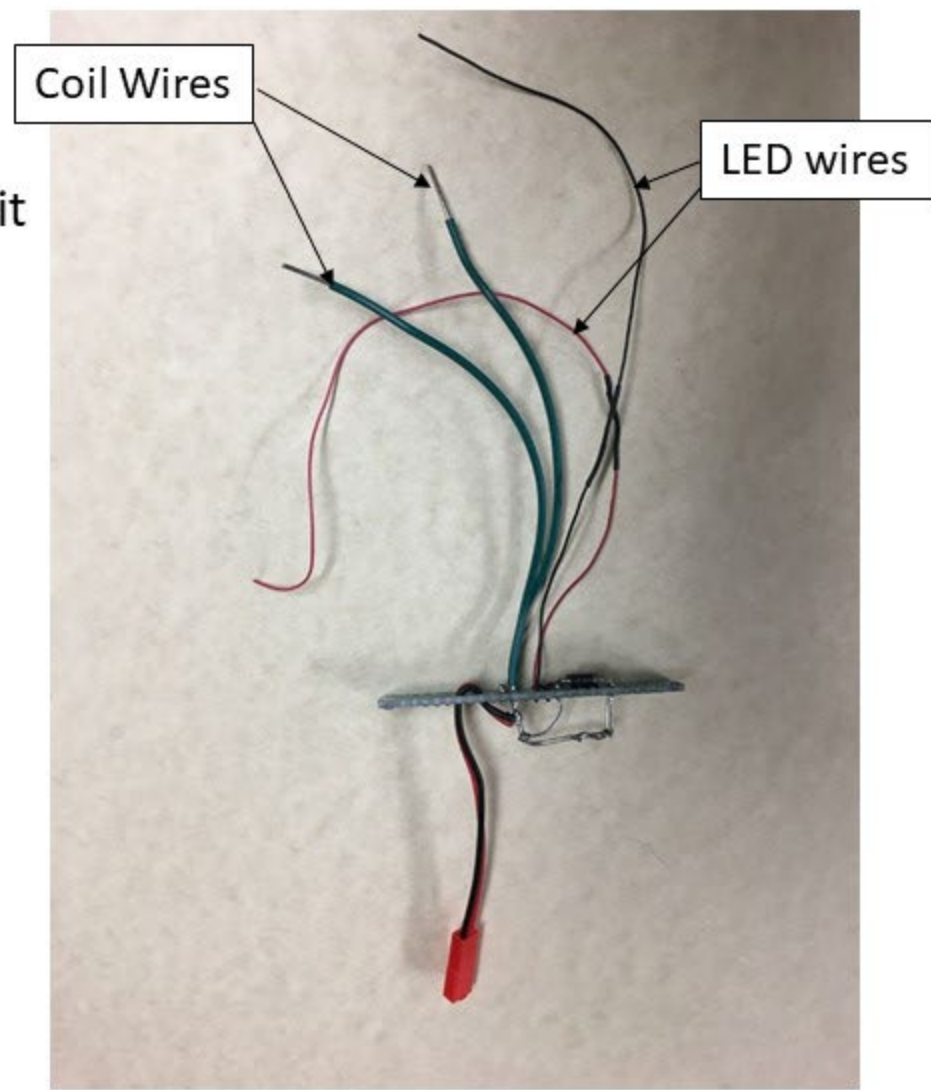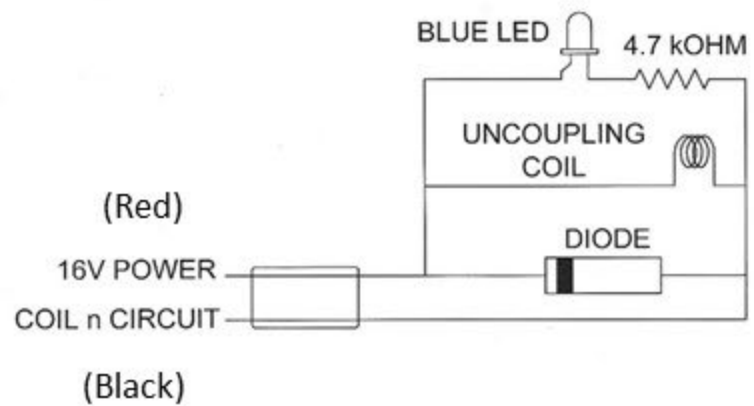



Uncoupling  
Coils

Suppression  
Circuits

Holes in  
subroadbed

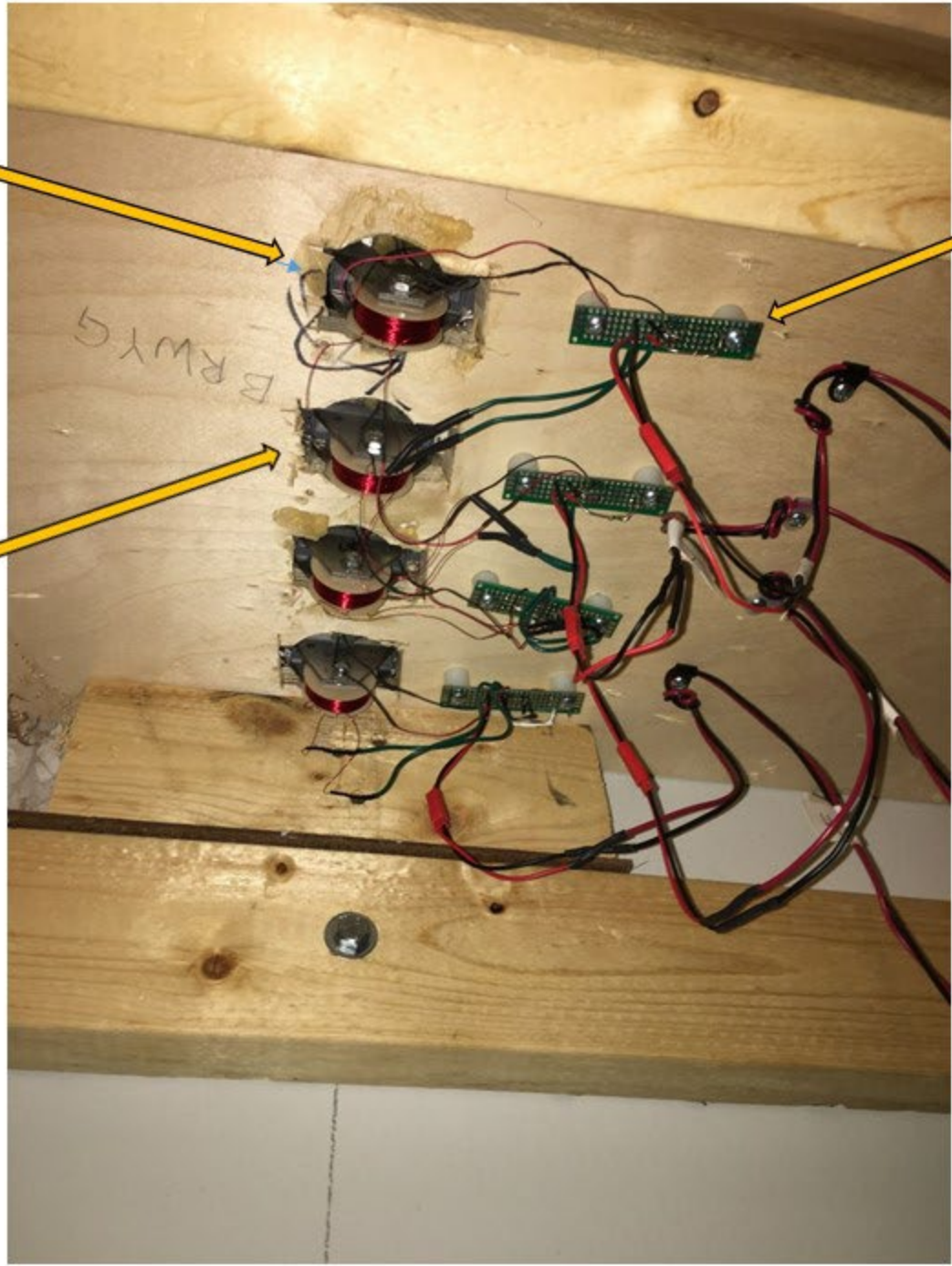4 pairs of  
wires go  
back to  
control  
circuit




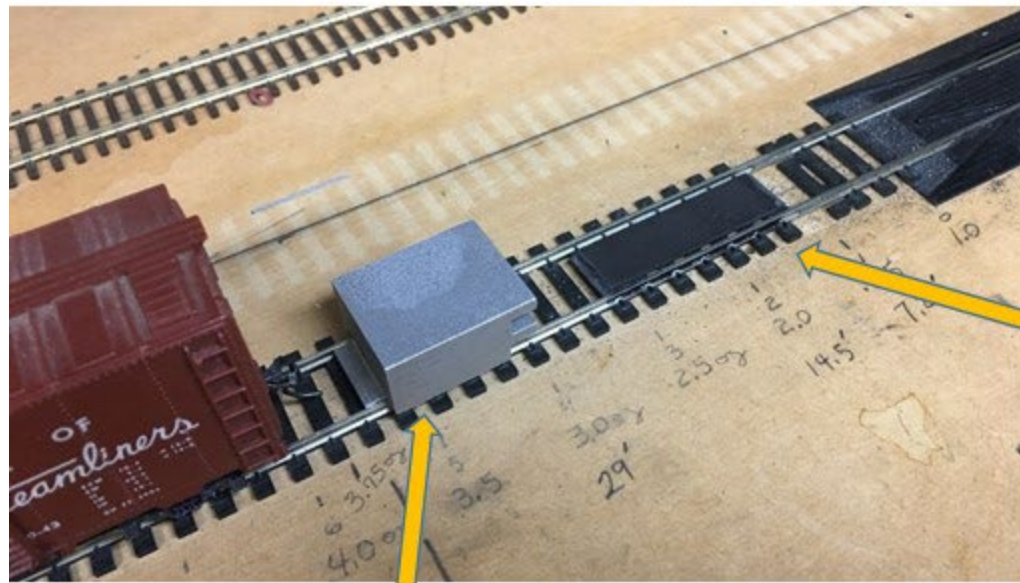


Permanent magnet uncoupler


Micro-Mark adjustment tool



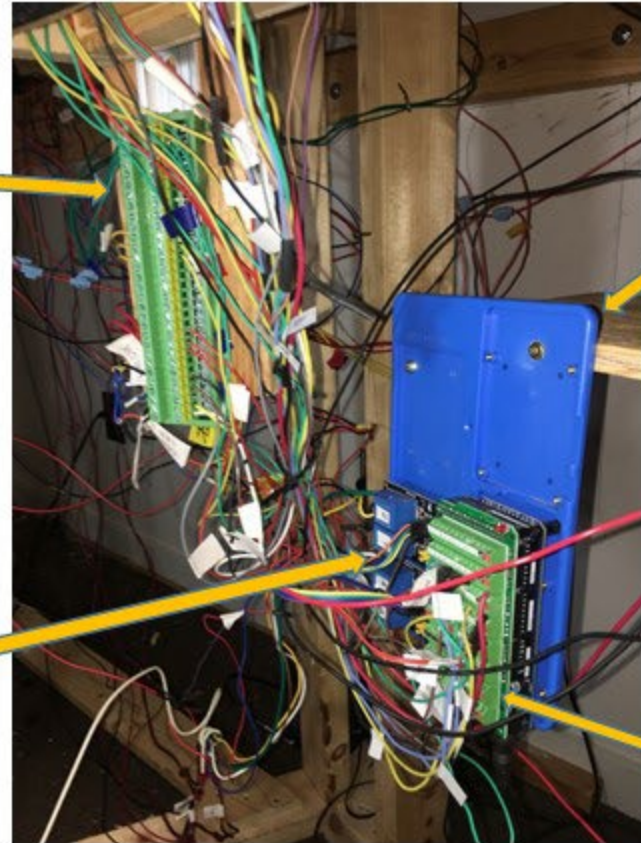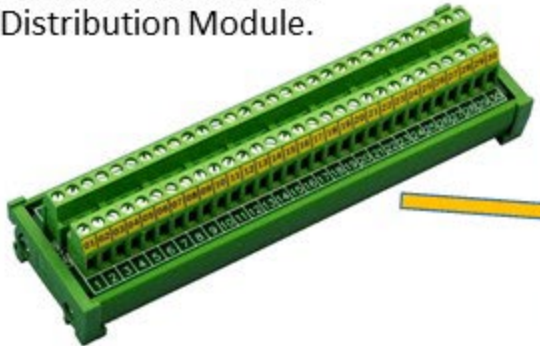Electronics-Salon DIN  
Rail Mount 30  
Position 24A / 400V  
Screw Terminal Block  
Distribution Module.



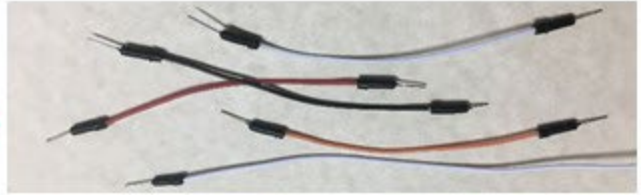UNIROI 7 in 1 RAB Holder  
Raspberry Pi Breadboard




Relays

Electronics-Salon Screw  
Terminal Block Breakout  
Module, for Arduino MEGA-  
2560 R3 (on top)



Arduino MEGA-2560 R3  
(on bottom)




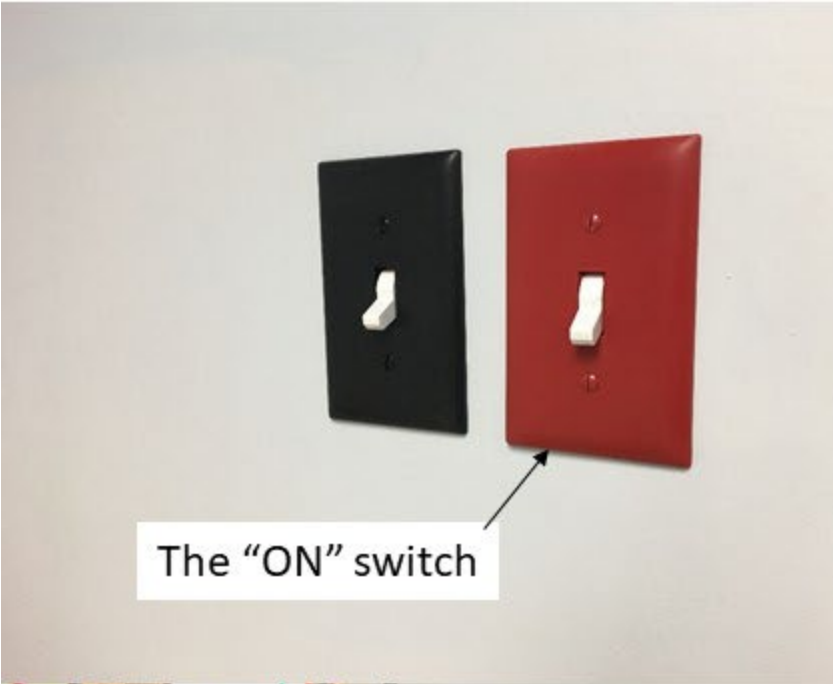

The "ON" switch



Uncoupler  
Power supply

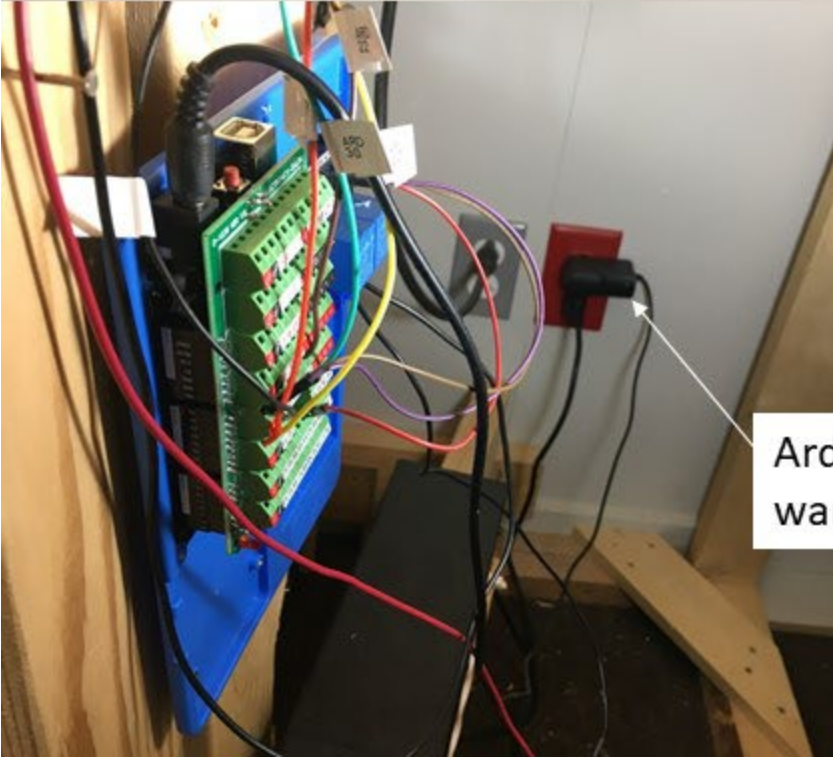

Arduino wall  
wart